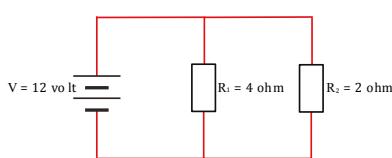


Finding the power dissipated by resistors in parallel



$$I_1 = \frac{V}{R_1}$$

$$= \frac{12 \text{ volt}}{4 \text{ ohm}}$$

$$= 3 \text{ ampere}$$

$$I_2 = \frac{V}{R_2}$$

$$= \frac{12 \text{ volt}}{2 \text{ ohm}}$$

$$= 6 \text{ ampere}$$

$$I = I_1 + I_2$$

$$= 3 \text{ ampere} + 6 \text{ ampere}$$

$$= 9 \text{ ampere}$$

$$P_1 = I_1 \times V$$


$$= 3 \text{ ampere} \times 12 \text{ volt}$$

$$= 36 \text{ watt}$$

$$P_2 = I_2 \times V$$

$$= 6 \text{ ampere} \times 12 \text{ volt}$$

$$= 72 \text{ watt}$$

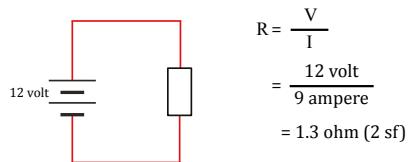

$$R = \frac{V}{I}$$

$$= \frac{12 \text{ volt}}{9 \text{ ampere}}$$

$$= 1.3 \text{ ohm (2 sf)}$$

$$P = V \times I$$

$$= 12 \text{ volt} \times 9 \text{ ampere}$$

$$= 108 \text{ watt}$$

$$P = P_1 + P_2$$

$$= 72 \text{ watt} + 36 \text{ watt}$$

$$= 108 \text{ watt}$$