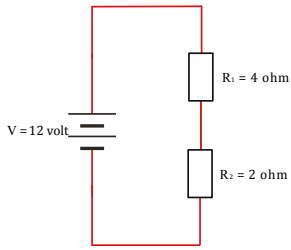



Finding the the power dissipated by resistors in series



$$R = R_1 + R_2$$

$$= 4 \text{ ohm} + 2 \text{ ohm}$$

$$= 6 \text{ ohm}$$

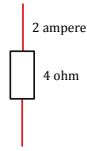

$$V_1 = R_1 \times I$$


$$= 4 \text{ ohm} \times 2 \text{ ampere}$$

$$= 8 \text{ volts}$$

$$P_1 = V_1 \times I$$

$$= 8 \text{ volt} \times 2 \text{ ampere}$$


$$= 16 \text{ watt}$$

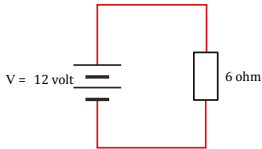

$$I = \frac{V}{R}$$

$$= \frac{12 \text{ volt}}{6 \text{ ohm}}$$

$$= 2 \text{ ampere}$$

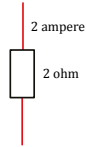

$$V_2 = R_2 \times I$$

$$= 2 \text{ ohm} \times 2 \text{ ampere}$$

$$= 4 \text{ volt}$$

$$P_2 = V_2 \times I$$

$$= 4 \text{ volt} \times 2 \text{ ampere}$$

$$= 8 \text{ watt}$$

$$P = V \times I$$

$$= 12 \text{ volt} \times 2 \text{ ampere}$$

$$= 24 \text{ watt}$$

$$P = P_1 + P_2$$

$$= 16 \text{ watt} + 8 \text{ watt}$$

$$= 24 \text{ watt}$$

IOP Institute of Physics

Calculation of the power dissipated by resistors in series

This document is a part of Supporting Physics Teaching, from the Ee topic, episode number 02, and the PN thread.

A gentle reminder that it for private and institutional use only.

The location



<http://supportingphysicsteaching.net/>