

a single, simple loop

analyse circuits in complete electrical loops

voltage
(drives the flow)

electrical current
(rate of flow of charge)

resistance
(impedes the flow)

current is always the dependent variable

useful because electrical circuits are good at controlled long range working

resistance and more complex circuits

resistance depends on circuit element

resistance depends on number of circuit elements in loop

series connections: 1 loop

parallel connections: >1 loop

resistance varies with the arrangement of the loops and what you put in them

a fruitful model

electrical working

mechanical loops give tangible experiences

mechanical working

energy and power

energy in

energy out

chemical store

thermal store

kinetic store

gravitational store

using power is often more natural than using energy

power in

power out

particularly useful for thinking about light bulbs