
 


A simple circuit: one loop

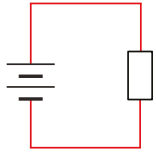Measure and calculate for series connections



Copy the circuit and show where you placed your meters

Record your measurements

V = volt

I = ampere

Calculate the power


$P = V \times I$

= volt × ampere

= watt

A circuit with series connections: still one loop

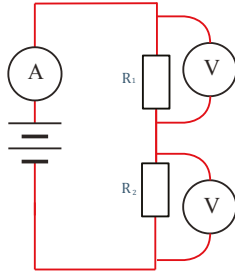Measure and calculate for series connections



Calculate the power dissipated in each resistor

$$\begin{aligned} P_1 &= V_1 \times I \\ &= \text{volt} \quad \times \text{ampere} \\ &= \text{watt} \end{aligned}$$

$$\begin{aligned} P_2 &= V_2 \times I \\ &= \text{volt} \quad \times \text{ampere} \\ &= \text{watt} \end{aligned}$$

Record your measurements

$$V_1 = \text{volt}$$

$$V_2 = \text{volt}$$

$$I = \text{ampere}$$

Calculate the power dissipated in each resistor

$$\begin{aligned} P &= P_1 + P_2 \\ &= \text{watt} + \text{watt} \\ &= \text{watt} \end{aligned}$$