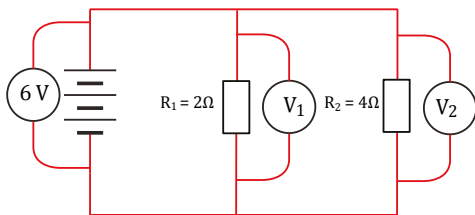


# Parallel connections question 1

In this circuit, a 6 V battery is connected to two resistors in series.  
The resistance of  $R_2$  is bigger than the resistance of  $R_1$ .



What are the readings on voltmeters  $V_1$  and  $V_2$ ? Tick ONE box (✓)


	voltmeter $V_1$	voltmeter $V_2$
<input type="checkbox"/>	4 V	2 V
<input type="checkbox"/>	2 V	4 V
<input type="checkbox"/>	3 V	3 V
<input type="checkbox"/>	6 V	6 V
<input type="checkbox"/>	12 V	24 V
<input type="checkbox"/>	3 V	1.5 V

How confident are you that your answers to this question are correct?  
Tick ONE box (✓)

Very confident  Fairly confident  Not confident  Just guessing
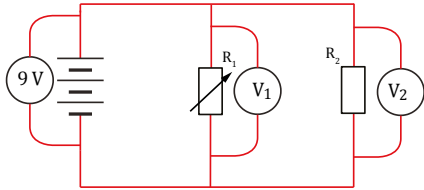
# Parallel connections question 2

In this circuit, a 6 V battery is connected to two resistors in series.  
The resistance of  $R_1$  is bigger than the resistance of  $R_2$ .



How confident are you that your answers to this question are correct?  
Tick ONE box (✓)

Very confident  Fairly confident  Not confident  Just guessing

(a) What happens to the reading on voltmeter  $V_1$ ?  
Tick ONE box (✓)

- It gets bigger.
- It stays the same.
- It gets smaller.

(b) What happens to the reading on voltmeter  $V_2$ ?  
Tick ONE box (✓)


- It gets bigger.
- It stays the same.
- It gets smaller.

(b) How would you explain this? Tick ONE box (✓)

- As  $R$  increases, the voltage across it gets bigger (because  $V = I \times R$ ). The other voltmeter is across a fixed resistance, so it stays the same.
- As  $R$  increases, the voltage across it gets bigger (because  $V = I \times R$ ). The sum of the two voltages has to be equal to the supply voltage. So the voltage across the other resistor gets smaller.
- Both resistors are connected directly across the power supply, so the readings on both voltmeters are equal to the supply voltage.
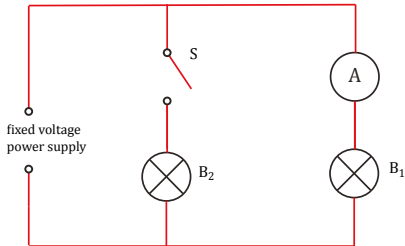
# Parallel connections question 3

In this circuit, the power supply has a fixed voltage output.  
 Switch S is open.  
 Bulb  $B_1$  is lit.  
 There is a reading on the ammeter.



How confident are you that your answers to this question are correct?  
 Tick ONE box (✓)

- Very confident    Fairly confident    Not confident    Just guessing
- 

(a) What happens to the reading on ammeter?  
 Tick ONE box (✓)

- It gets bigger.  
 It stays the same.  
 It gets smaller.

(b) What happens to the brightness of bulb  $B_1$ ?  
 Tick ONE box (✓)

- It gets brighter.  
 It stays the same brightness.  
 It gets dimmer.

(b) How would you explain this? Tick ONE box (✓)

- Some of the current now goes through  $B_2$ , bypassing  $B_1$ .  
 Two bulbs need a bigger current from the power supply.  
 The voltage across each parallel branch stays the same.  
 The total resistance is now bigger, so the current gets less.

Other (please explain): \_\_\_\_\_


# Parallel connections question 4

In each of these circuits, two resistors are connected in parallel to a battery.  
 The resistance of each resistor is shown.  
 All the meters are ammeters. The readings on some of the ammeters are shown.  
 Write down the readings you would expect to see on the other ammeters.

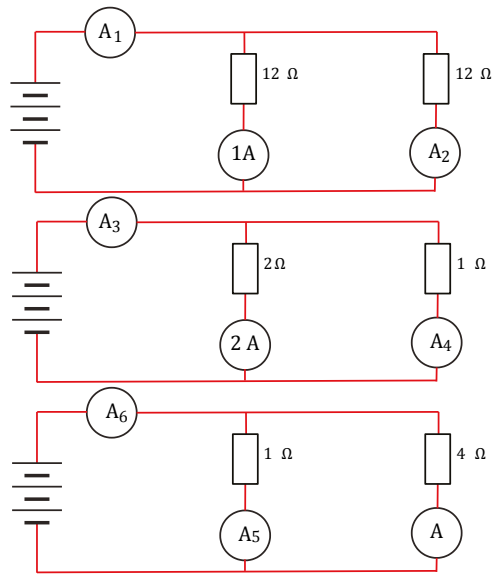- (a) The reading on ammeter  $A_1$  is \_\_\_ ampere
- (b) The reading on ammeter  $A_2$  is \_\_\_ ampere
- (c) The reading on ammeter  $A_3$  is \_\_\_ ampere
- (d) The reading on ammeter  $A_4$  is \_\_\_ ampere
- (e) The reading on ammeter  $A_5$  is \_\_\_ ampere
- (f) The reading on ammeter  $A_6$  is \_\_\_ ampere

How confident are you that your answers to this question are correct?  
 Tick ONE box (✓)

- Very confident    Fairly confident    Not confident    Just guessing
- 



# Answers

## Question 1

The potential difference across both resistors in a parallel circuit is the same, irrespective of resistance (the current through each resistor is different).

## Question 2

This is just the same as question 1.

## Question 3

When the switch is closed, the ammeter reading stays the same, as does the bulb brightness. This is because the potential difference across  $B_1$  stays the same.

## Question 4

$A_1$  is 2 ampere.  $A_2$  is 1 ampere (current equal in equal arms);

$A_3$  is 6 ampere and  $A_4$  is 4 ampere (current inversely proportional to resistance. Big resistance, small current);

$A_5$  is 4 ampere (current inversely proportional to resistance) and  $A_6$  is 5 ampere.