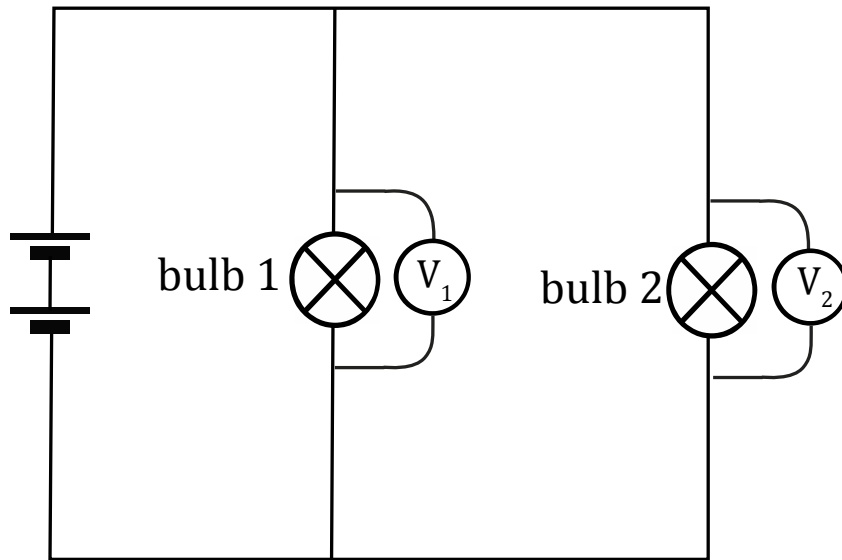


Predict, then measure



Measure voltage across battery = ____ volt

Predict voltage (V_1) = ____ volt

Predict voltage (V_2) = ____ volt

Measure voltage (V_1) = ____ volt

Measure voltage (V_2) = ____ volt